

<b>Name:</b>	 <b>UPES</b> UNIVERSITY WITH A PURPOSE
<b>Enrolment No:</b>	

**UNIVERSITY OF PETROLEUM AND ENERGY STUDIES**  
**End Semester Examination, December 2020**

<b>Course:</b> Network Analysis <b>Program:</b> B. Tech- Electronics and Communication Engineering <b>Course Code:</b> ECEG -2020	<b>Semester:</b> III <b>Time</b> 03 hrs. <b>Max. Marks:</b> 100
---	---

**Instructions:** (i) Answer all the questions.

**SECTION A (30 Marks)**


**Each Question will carry 5 Marks**  
**Instruction: Write briefly (5-6 lines)**





S. No	Question	CO
Q 1	What do you mean by two-port network systems and differentiate two-port and one-port network systems? Explain with appropriate applications.	CO2
Q 2	Briefly define for: (i) Graph (ii) Node (iii) Tree	CO3
Q 3	Define Hurwitz polynomial and write its properties.	CO4
Q 4	Explain the duality property of Thevenin's and Norton's theorem. Also write a statement of Thevenin's theorem.	CO1
Q 5	Explain the condition of Reciprocity and symmetry two-port network system with the significance also.	CO2
Q 6	Write the necessary conditions for transfer functions. Differentiate the impedance transfer function and admittance functions.	CO3

**SECTION B (50 Marks)**

**Each question will carry 10 marks**  
**Instruction: Attempt all the questions**

Q 1	Find the Norton equivalent circuit for the network external to the $9\Omega$ resistor in Figure.	<b>CO1</b>
-----	--	------------

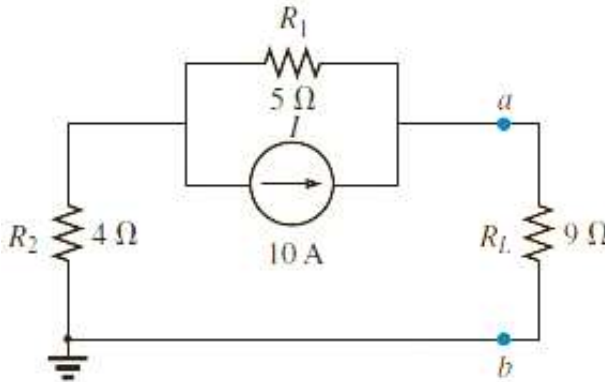

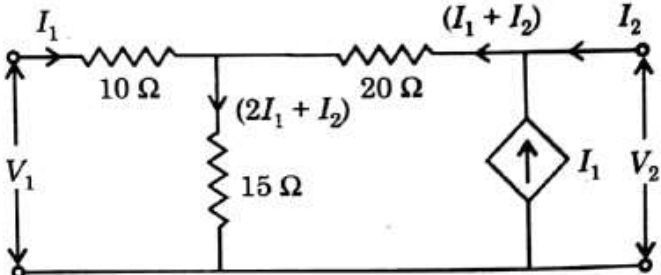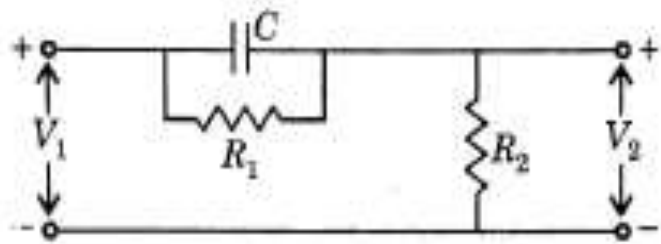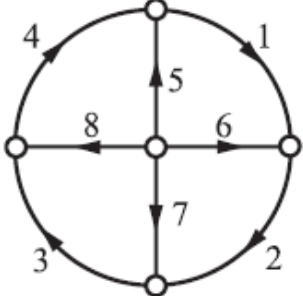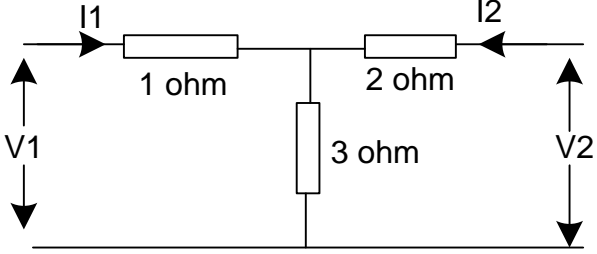Q 2	<p>Determine the Z-parameters of network shown in Figure.</p> 	CO2
Q 3	<p>Find driving point impedance <math>Z_{11}(s)</math> and voltage transfer function <math>G_{21}(S) = \frac{V_2(s)}{V_1(s)}</math> of the given network circuit.</p> 	CO3
Q 4	<p><b>Attempt both the parts</b>  (a) Determine Tie-set matrix of the give directed graph of electrical network.</p>  <p>(b) Check the whether the given polynomial function are Hurwitz or not?</p> $P(s) = s^4 + s^3 + 5s^2 + 3s + 4$	CO4
Q 5	<p>For the network shown in figure. Calculate (i) Z parameters (ii) Y parameters</p> 	CO2

### SECTION-C


**Each Question carries 20 Marks.**

**Instruction: Write long answer.**

Q 1

**Attempt both the parts:**

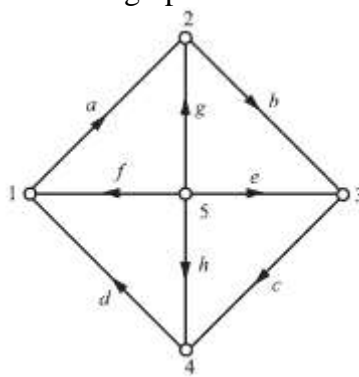(a) Design all the possible trees and verify the number of tree using mathematical analysis. Also, determine the incidence matrix for graph.



(b) An impedance function is given by

$$Z(s) = \frac{(s + 4)(s + 6)}{(s + 3)(s + 5)}$$

Design the one port R-C representation of circuit for (i) Cauer-I (ii) Cauer- II forms.

**CO4**

**(10+10)**

\*\*\*\*\*