


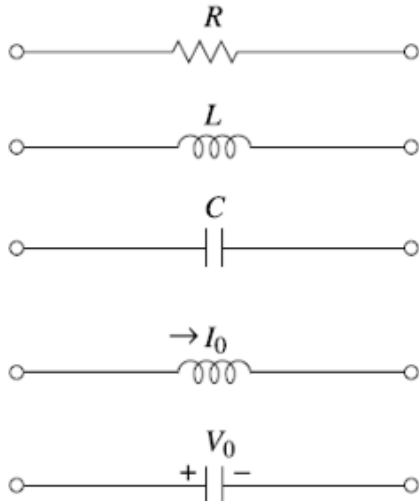
| | |
|--------------------------------------|--|
| Name: Enrolment No: |  |
|--------------------------------------|--|




UNIVERSITY OF PETROLEUM AND ENERGY STUDIES
End Semester Examination, December 2022


Course: Electrical Circuit Analysis **Semester: III**
Program: B.Tech (EE) **Time: 03 hrs.**
Course Code: EPEG2009 **Max. Marks: 100**

Instructions: Read the instructions provided for every question properly before attempting the answer. Use of calculator is permitted.

SECTION A
(5Qx4M=20Marks)

| S. No. | | Marks | CO |
|--------|--|-------|-----|
| Q 1 | Explain with suitable diagram the two Kirchhoff's Law. | 4 | CO1 |
| Q 2 | Evaluate the Laplace transform of: (a) $u(t) = 1$ $t > 0$ $u(t) = 0$ $t < 0$ (b) $r(t) = t$ $t > 0$ $r(t) = 0$ $t < 0$ | 4 | CO4 |
| Q 3 | Test results for a two-port network are (a) $I_1 = 0.1 \angle 0^\circ$ A, $V_1 = 5.2 \angle 50^\circ$ V, $V_2 = 4.1 \angle -25^\circ$ V with Port 2 open circuited (b) $I_2 = 0.1 \angle 0^\circ$ A, $V_1 = 3.1 \angle -80^\circ$ V, $V_2 = 4.2 \angle 60^\circ$ V, with Port 1 open circuited. Find Z parameters. | 4 | CO5 |
| Q 4 | Draw the equivalent circuit at $t = 0^+$ of the elements with initial conditions as given below: <div style="text-align: center;">  </div> | 4 | CO2 |
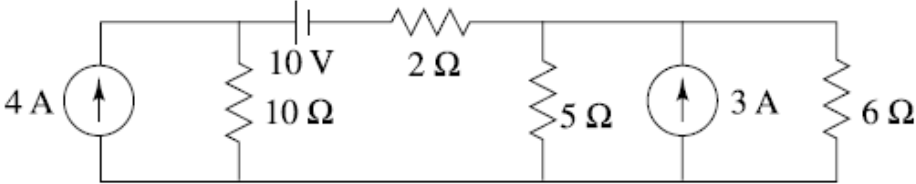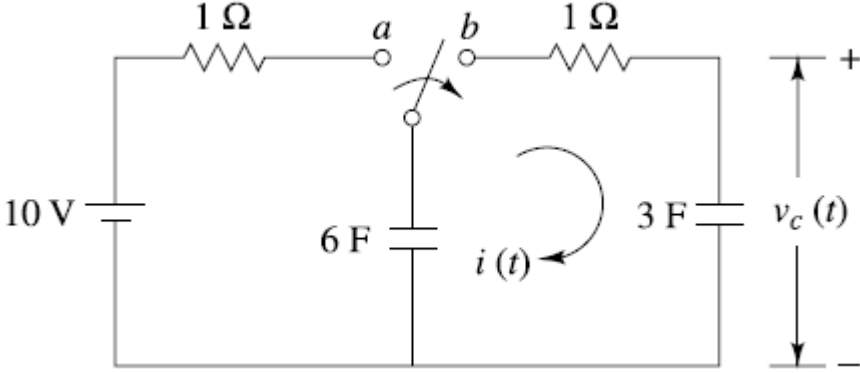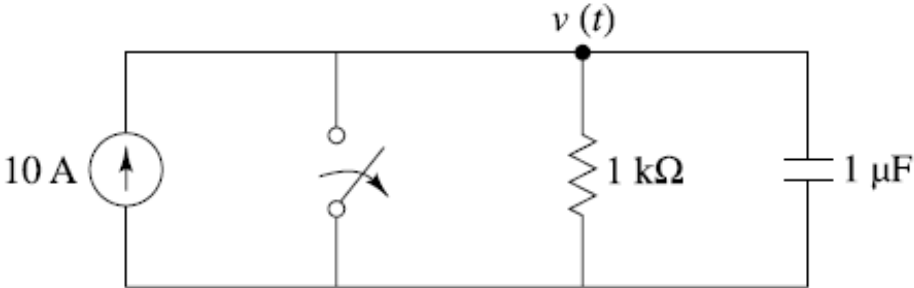
| | | | |
|---|--|----|-----|
| Q 5 | Explain the advantages of a three-phase system. | 4 | CO3 |
| SECTION B (4Qx10M= 40 Marks) | | | |
| Q 6 | Find the current through the 6Ω resistor using superposition theorem.  | 10 | CO1 |
| Q 7 | Explain two-wattmeter method along with the phasor diagram and how it can be used to measure three-phase power. | 10 | CO3 |
| Q 8 | In the network of figure below, the switch is moved from a to b at $t = 0$. Determine $i(t)$ and $v_c(t)$.  | 10 | CO4 |
| Q 9 | In the network shown in figure below, the switch is opened at $t = 0$. Solve for v , $\frac{dv}{dt}$ and $\frac{d^2v}{dt^2}$ at $t=0^+$.  <p style="text-align: center;">OR</p> In the network shown in Figure below, the switch is changed from the position 1 to the position 2 at $t = 0$, steady condition having reached before switching. Find the values of i , $\frac{di}{dt}$ and $\frac{d^2i}{dt^2}$ at $t=0^+$. | 10 | CO2 |

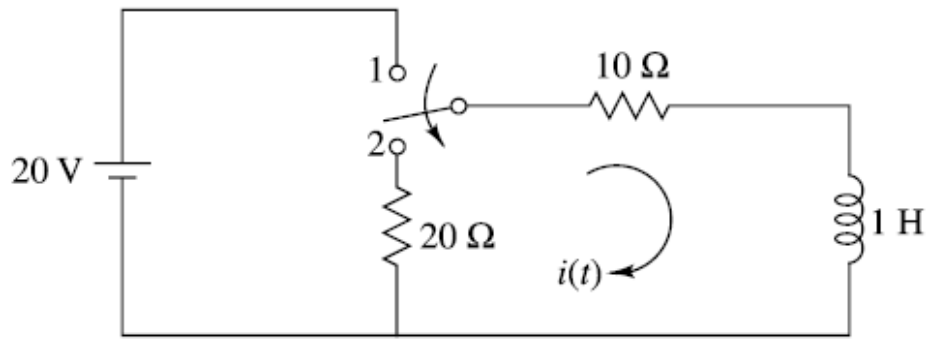

SECTION-C
(2Qx20M=40 Marks)

Q 10 Derive the expression of real, reactive and apparent power along with the phasor diagram (lagging power factor) of a three-phase balanced star connected load. 20 CO3

Q 11 The switch in figure below is opened at time $t = 0$. Determine the voltage $v(t)$ for $t > 0$.

OR

The network shown in figure below was initially in the steady state with the switch in the position a. At $t = 0$, the switch goes from a to b. Find an expression for voltage $v(t)$ for $t > 0$.

20 CO4