


| Name:   |   |  |     |
|---|---|--|-----|
| Enrolment No:   |   |  |     |
| <b>UNIVERSITY OF PETROLEUM AND ENERGY STUDIES</b><br><b>End Semester Examination, May 2022</b>                                  |   |  |     |
| <b>Course: Electrical Drives</b><br><b>Program: B.tech. Electrical</b><br><b>Course Code: EPEG 3012</b><br><b>Instructions:</b> |   | <b>Semester: VI</b><br><b>Time : 03 hrs.</b><br><b>Max. Marks:100</b>              |     |
| <b>SECTION A</b><br><b>(5Qx4M=20Marks)</b>  |   |  |     |
| S. No.  |   | Marks  | CO  |
| Q 1   | What do you understand by soft start? Name the soft start methods employed for induction motors.  | 4  | CO2 |
| Q.2   | Why DC motor should not be employed on lightly loaded or no-loaded conditions?  | 4  | CO1 |
| Q.3   | State the advantages of the Electrical Drives.  | 4  | CO1 |
| Q.4   | Describe the components of the load torque.   | 4  | CO1 |
| Q.5   | Which DC drive is known as constant speed drives? Justify your answer.  | 4  | CO1 |
| <b>SECTION B</b><br><b>(4Qx10M= 40 Marks)</b>   |   |  |     |
| Q.6   | Illustrate the power flow diagram for induction motor and derive the expression for rotor efficiency.   | 10   | CO3 |
| Q.7   | <p>A 220 V, 1200 rpm, 15A separately excited motor has armature resistance and inductance of 1.8 ohm and 32mH respectively. This motor is controlled by a single phase fully controlled rectifier with an ac source voltage of 230 V, 50Hz. Identify the modes and calculate speed for:</p> <p>(a) <math>\alpha = 45^\circ</math> and torque = 40 N-m</p> <p>(b) <math>\alpha = 45^\circ</math> and torque = 10 N-m</p> | 10   | CO4 |
| Q.8   | A 220 V, 24 A, 100 rpm, separately excited dc motor has an armature resistance of 2ohm. Motor is controlled by a chopper with frequency of 500Hz and source voltage of 230V. Calculate the duty ratio for 1.2   | 10   | CO3 |

|  |   |           |            |
|--|---|-----------|------------|
|  | times rated torque and 500 rpm.   |           |            |
| Q.9  | Explain the stator voltage control scheme to control the speed of induction motors and discuss its merits and demerits.   | <b>10</b> | <b>CO2</b> |
| <b>SECTION-C</b><br><b>(2Qx20M=40 Marks)</b> |   |           |            |
| Q.10   | <p>A 230V, 1000rpm, 30A separately excited motor has armature resistance and inductance of 0.7 ohm and 50mH respectively. Motor is controlled in regenerative braking by a chopper operating at 800Hz from a dc source of 230 V. assuming continuous conduction</p> <p>(i) Calculate duty ratio of chopper for rated torque and the speed of 800 rpm.</p> <p>(ii) What will be the motor speed for duty ratio of 0.6 and rated motor torque?</p> <p>(iii) What will be the maximum allowable speed of motor, if chopper has a maximum duty ratio of 0.9 and maximum allowable motor current is twice the rated current?</p> <p>(iv) Calculate power fed to the source for operating conditions in (iii)</p> | <b>20</b> | <b>CO3</b> |
| Q. 11  | <p>Explain the advantages of frequency-controlled induction motor. Why is the V/f ratio kept constant? draw the power circuit diagram and plot the torque slip curves.</p> <p style="text-align: center;"><b>OR</b></p> <p>Explain the slip power recovery system for induction motor drive. Also illustrate the Scherbius drive method for slip power recovery.</p>  | <b>20</b> | <b>CO4</b> |