

Name:
Enrolment No:

UPES

End Semester Examination, May 2024

Programme Name : B. Tech (Electronics and Computer)

Semester : II

Course Name : Analog Electronics-I

Time: 03 hrs

Course Code : ECEG1011

Max. Marks: 100

Nos. of page(s) : 3

Instructions: In Section B and C, one internal choice is provided for each.

SECTION A

Answer all questions.

S. No.		Marks	CO
Q 1	State the True/False (i) Bypass capacitors in an amplifier determine the high-frequency response. (ii) An octave corresponds to a doubling of the frequency. (iii) The drain current in a CS amplifier can be calculated using a Shockley equation. (iv) Base bias is less stable than voltage-divider bias.	4	CO1
Q 2	(i) In an FET, the trans-conductance g_m is proportional to (a) I_{DS} (b) I_{DS}^2 (c) $\sqrt{I_{DS}}$ (d) $\frac{1}{I_{DS}}$ (ii) A certain common-source amplifier has a voltage gain of 10. If the source bypass capacitor is removed, (a) the voltage gain will increase (b) the transconductance will increase (c) the voltage gain will decrease (d) the Q-point will shift. (iii) If the voltage gain doubles, the decibel voltage gain increased by (a) A factor of 2 (b) 3 dB (c) 6dB (d) 10 dB (iv) A Darlington transistor has (a) A very low input impedance (b) Three transistors (c) A very high current gain (d) One V_{BE} drop	4	CO1
Q 3	Describe the advantages and disadvantages of FET in comparison to BJT.	4	CO1
Q 4	A four identical amplifier has a lower 3 dB frequency for an individual stage of $f_L = 40\text{Hz}$. What is the value of f_L^* for this full amplifier.	4	CO4
Q 5	It desired to have a high gain amplifier with high input impedance and low output impedance. If a cascade of four stages is used, what configurations should be used for each stage?	4	CO4

SECTION B

Q 6	Show that the transconductance, g_m of a JFET is related to the drain current I_{DS} by $g_m = \frac{2}{ V_p } \sqrt{I_{DSS} I_D}$ If $V_p = -4\text{V}$ and $I_{DSS} = 4\text{mA}$, plot g_m versus I_D .	10	CO3
Q 7	Sketch the small-signal low frequency r_e model of a common emitter BJT configuration. Determine Z_i , Z_o , and A_v for the given configuration.	10	CO3
Q 8	Draw the Darlington pair circuit. Explain why the input impedance is higher than that of a single stage emitter follower.	10	CO4

OR

Calculate the dc bias voltages and currents for the Darlington configuration of Fig.1

 


Fig.1

Q 9 Sketch the transfer and drain characteristics of an n-channel JFET with $I_{DSS} = 9$ mA and $V_P = -6$ V for a range of $V_{GS} = -V_P$ to $V_{GS} = 0$ V.


10

CO2

SECTION C

Q 10 (i) Explain the construction of n-channel JFET.
(ii) Differentiate between (a) n-channel and p-channel MOSFET. (b) Depletion type and enhancement type MOSFET.
(iii) For the network of Fig.2, determine:
(a) V_{GSQ} and I_{DQ} .
(b) V_{DS} , V_D , V_G , and V_S .

Fig.2

 

5+5+10


CO2

Q 11 For the network of Fig.3
(a) Determine r_e .
(b) Find Z_i and Z_o .
(c) Calculate A_v .
(d) Repeat parts (b) and (c) with $r_o = 20$ k Ohm

4x5=20

CO3

Fig.3

 

OR

The self-bias configuration of Fig.4 has an operating point defined by $V_{GSQ} = -2.6$ V and $I_{DQ} = 2.6$ mA, with $I_{DSS} = 8$ mA and $V_P = -6$ V. The value of g_{os} is given as 20 mS.

- (a) Determine g_m .
- (b) Find r_d .
- (c) Find Z_i .
- (d) Calculate Z_o with and without the effects of r_d . Compare the results.
- (e) Calculate A_v with and without the effects of r_d . Compare the results.

5X4=20

 


Fig.4